
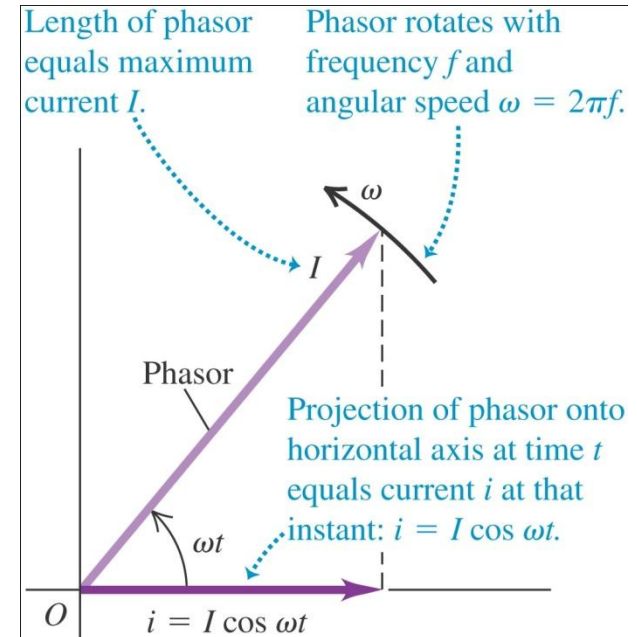


Chapter 21

Ac Circuits

AC current

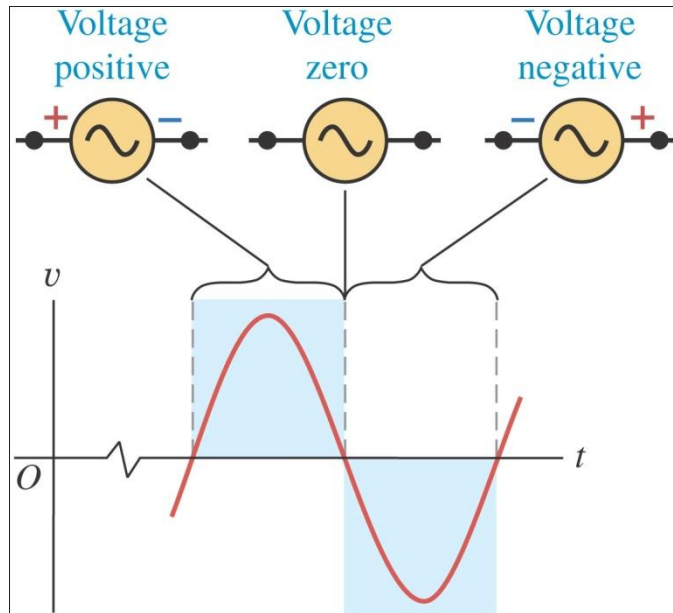

Transformer


Transforms AC voltage UP or DOWN

Historical basis for AC Grid your use

George Westinghouse (AC) vs Edison (DC)

Losses due to resistance in wire and eddy currents in transformer "core"

Typ eff ~ 95-99%


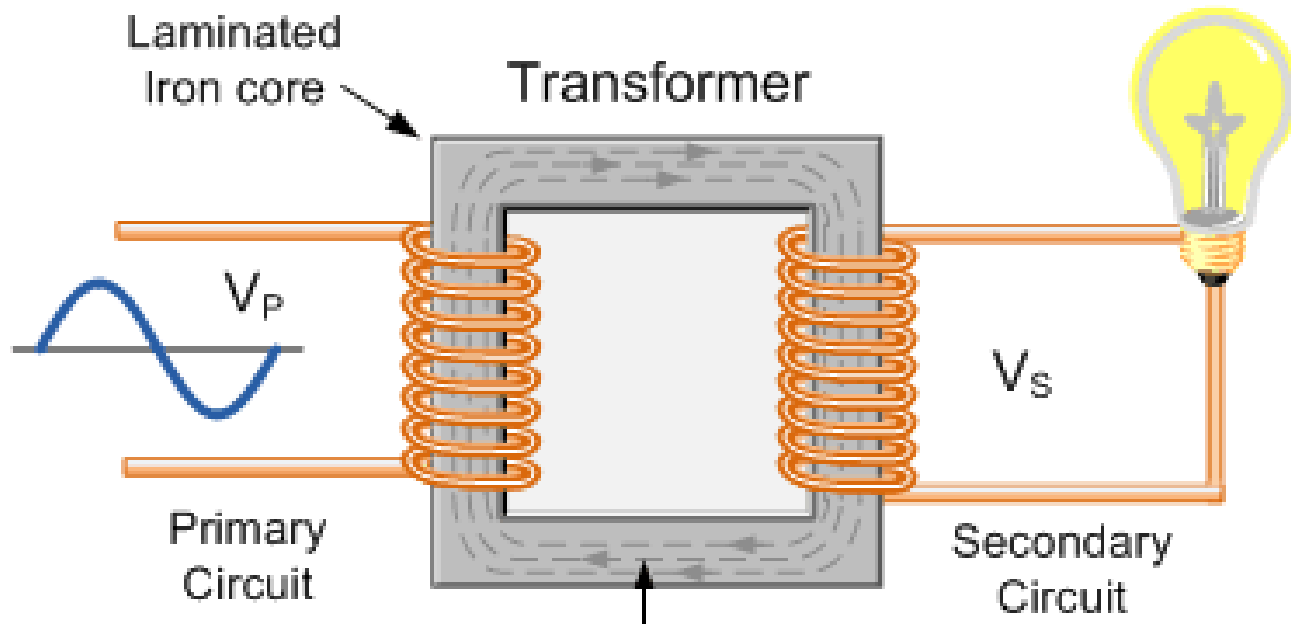


Magnetic Flux concentrated
in the Iron core produces
Eddy Currents which oppose it

Transformers


The induced emf *per turn* is the same in both coils, so we adjust the ratio of terminal voltages by adjusting the ratio of turns:

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

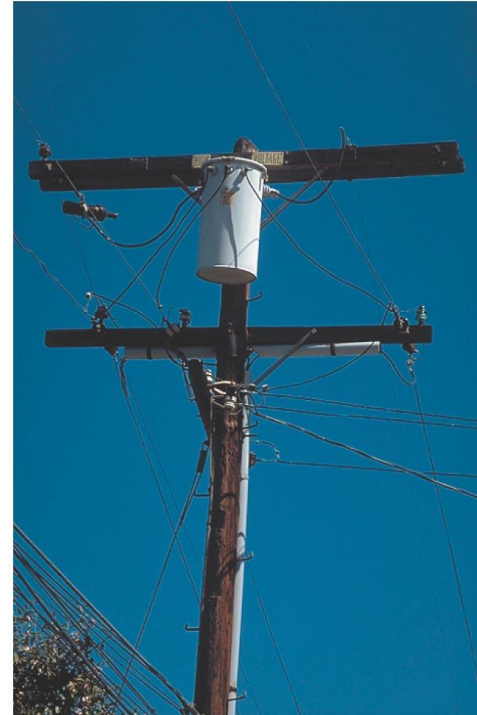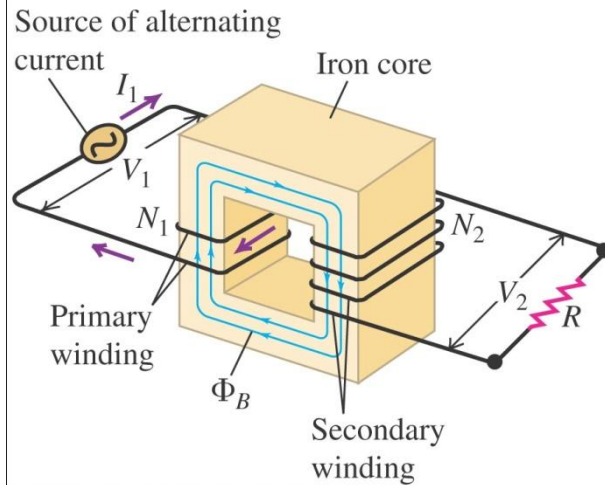


Transformers II


Schematic transformer

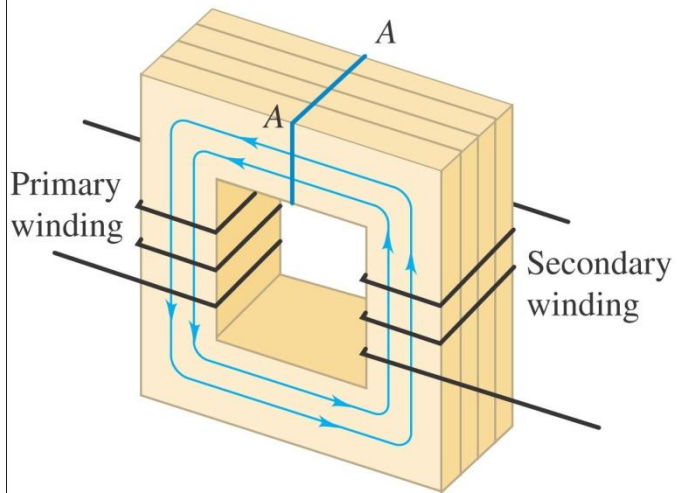



Large eddy currents in solid core

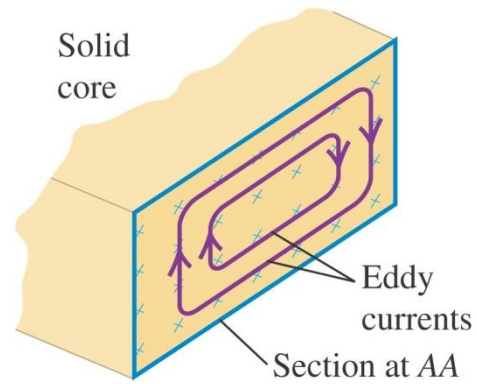


Smaller eddy currents in laminated core

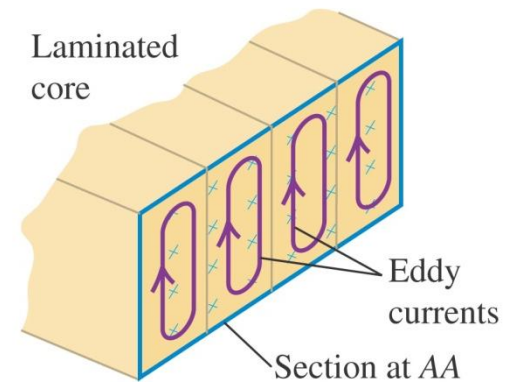

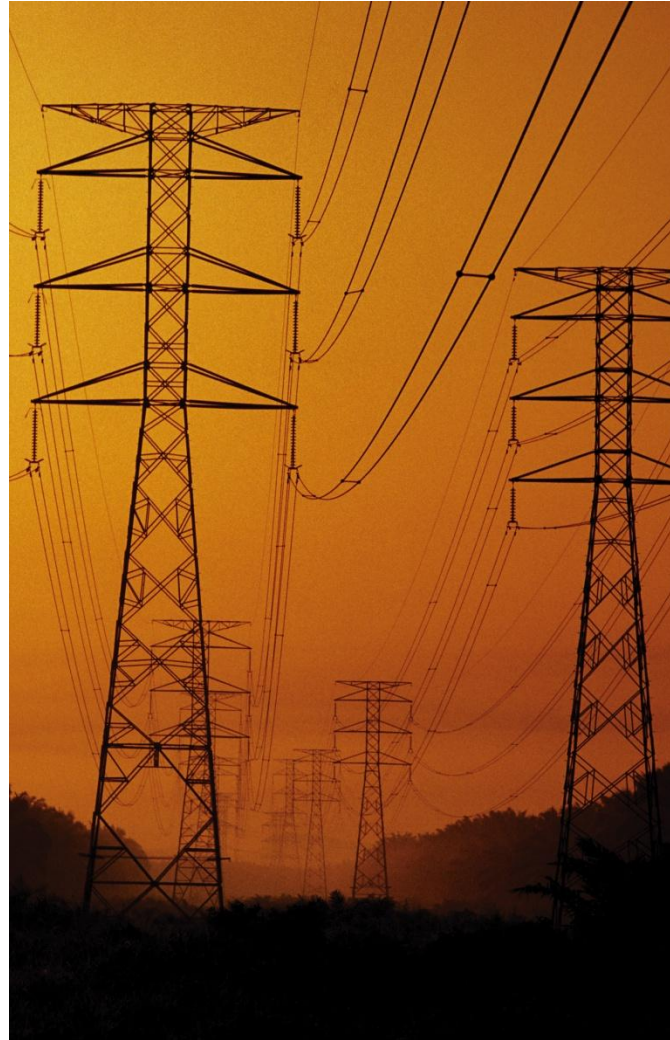

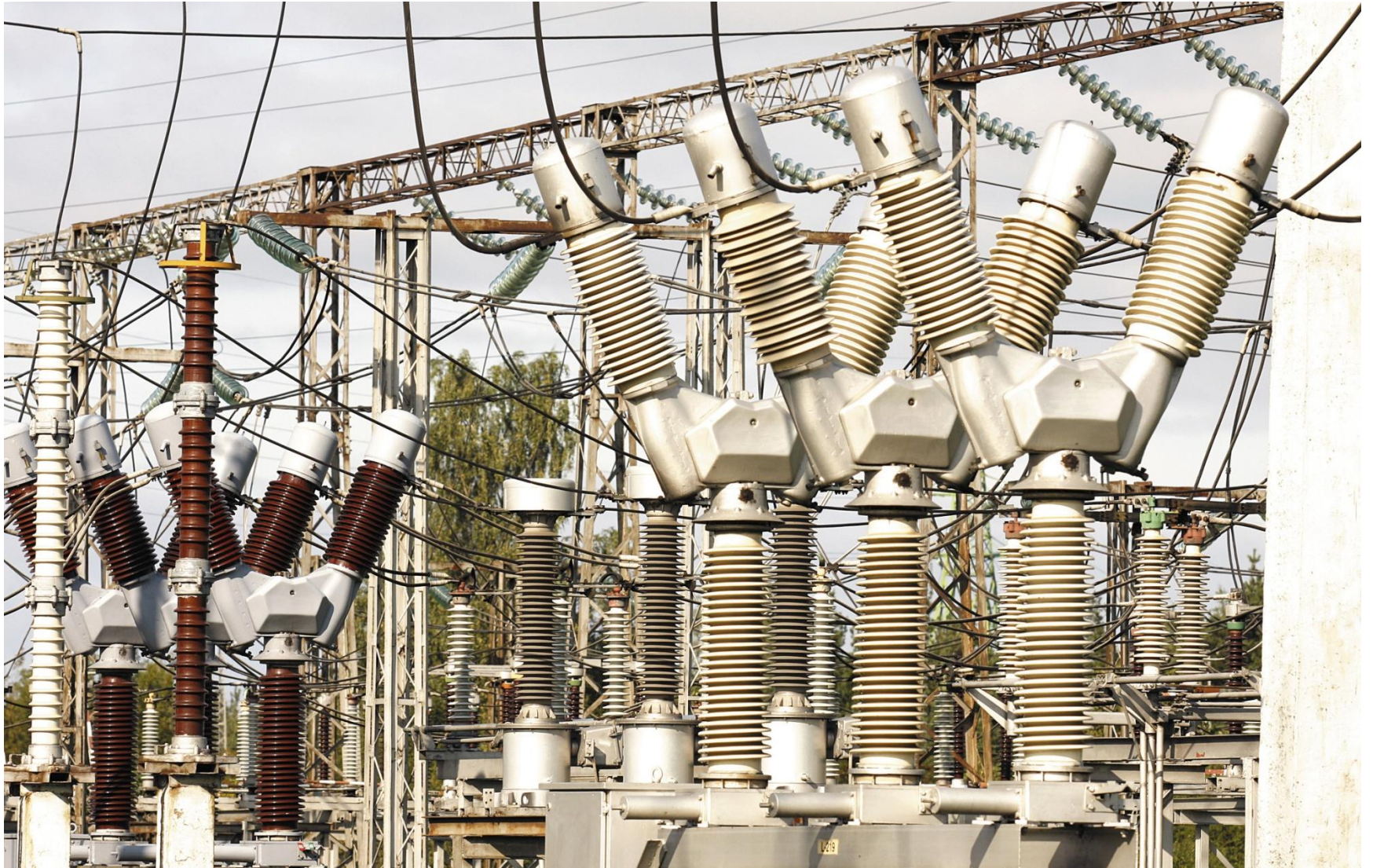

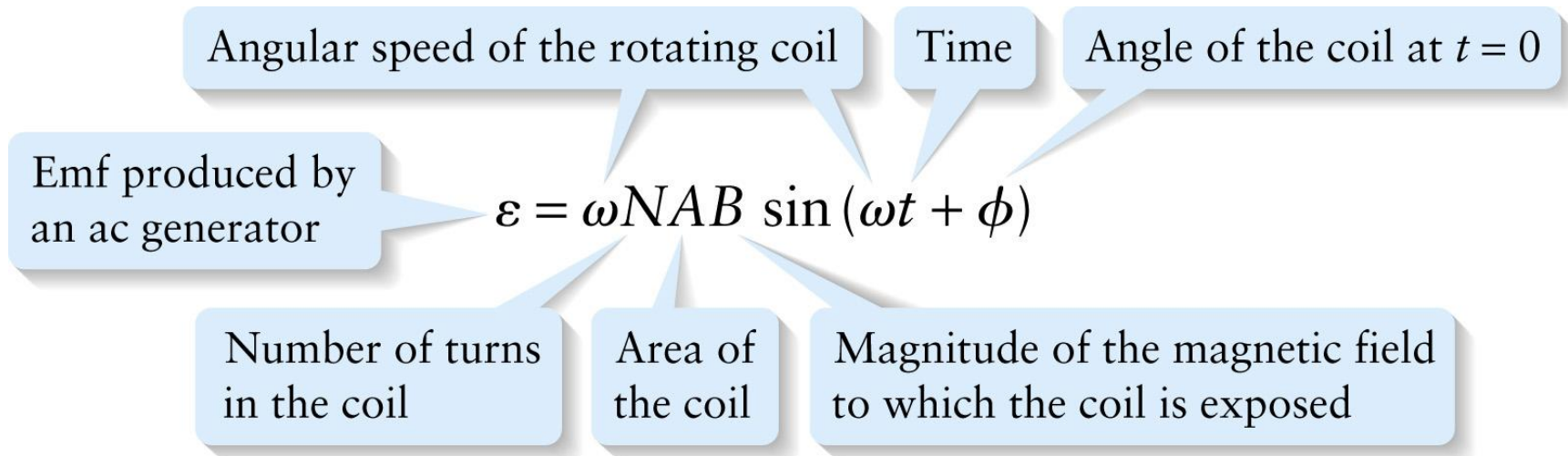

Time-varying voltage
provided by an ac source

Angular frequency
of the voltage

$$V(t) = V_0 \sin \omega t$$


Time

Voltage amplitude = maximum positive value of $V(t)$

The value V of this ac voltage oscillates between V_0 (the voltage amplitude) and $-V_0$.

The period T of this ac voltage equals the reciprocal of the frequency f :
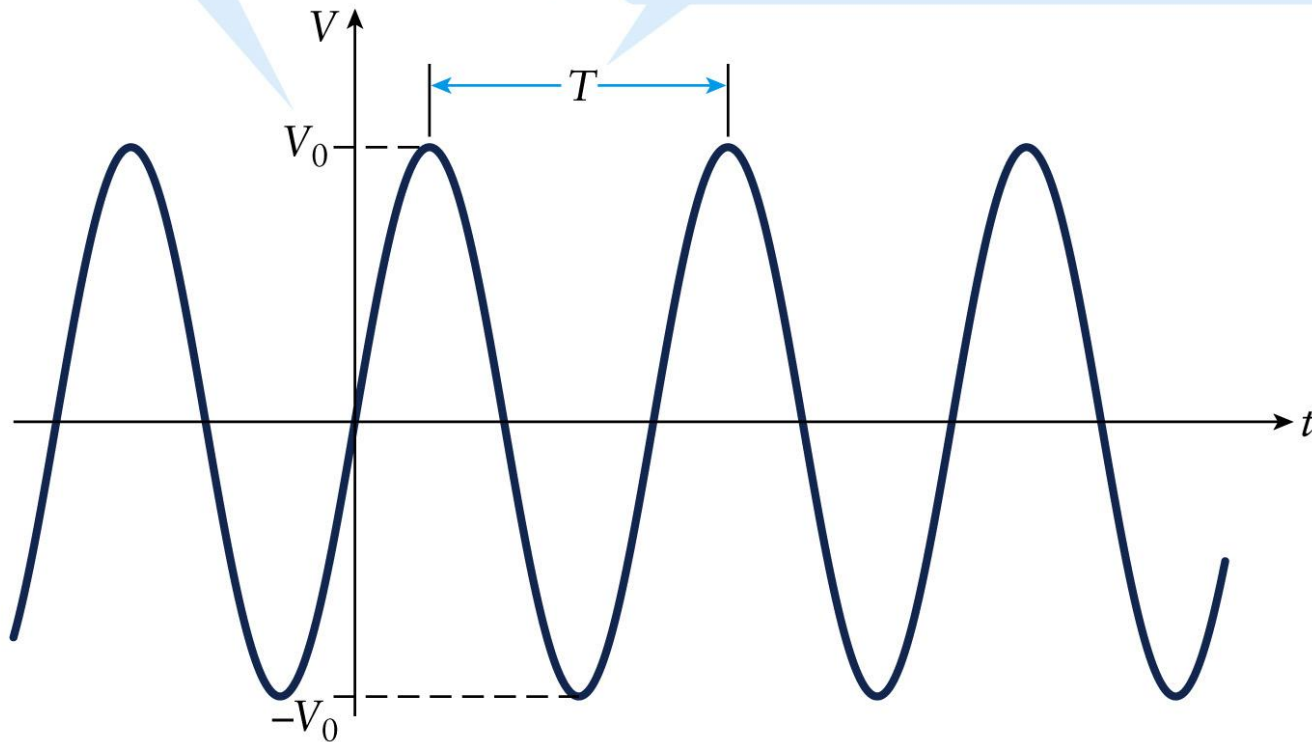
$$T = \frac{1}{f} = \frac{2\pi}{\omega}$$



Power into a resistor

Current through the resistor

$$P = i^2 R = \frac{V^2}{R}$$

Voltage across the resistor

Resistance of the resistor

The root mean square (rms) value of $V(t)$...

... is the square root of the average value of $V^2(t)$.

$$V_{\text{rms}} = \sqrt{(V^2(t))_{\text{average}}} = \frac{V_0}{\sqrt{2}}$$

If $V(t)$ is a sinusoidal function, its rms value equals the maximum value of $V(t)$ (the amplitude) divided by $\sqrt{2}$.

The root mean square (rms) value of $V(t)$...

... is the square root of the average value of $V^2(t)$.


$$V_{\text{rms}} = \sqrt{(V^2(t))_{\text{average}}} = \frac{V_0}{\sqrt{2}}$$

If $V(t)$ is a sinusoidal function, its rms value equals the maximum value of $V(t)$ (the amplitude) divided by $\sqrt{2}$.


A full-wave rectifier circuit

Meaning of the rms value of a sinusoidal quantity (here, ac current with $I = 3\text{ A}$):

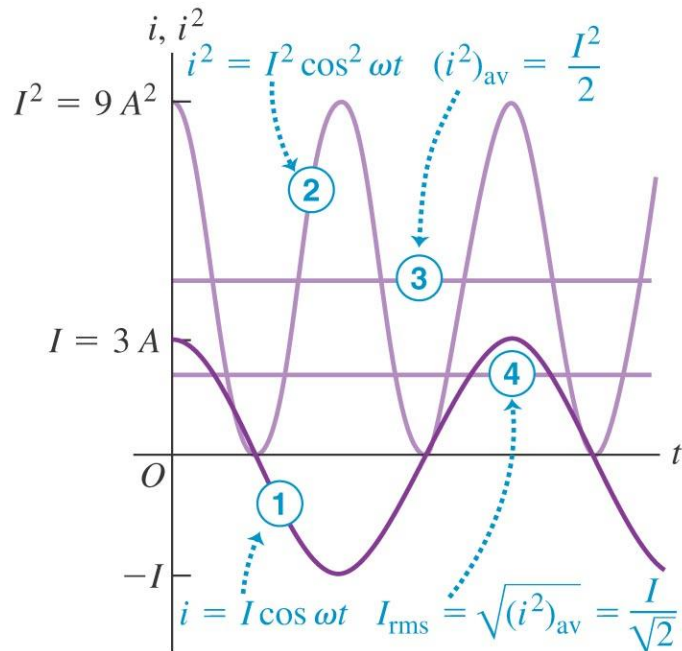
- ① Graph current i versus time.
- ② Square the instantaneous current i .
- ③ Take the *average* (mean) value of i^2 .
- ④ Take the *square root* of that average.



(a) A full-wave rectifier circuit

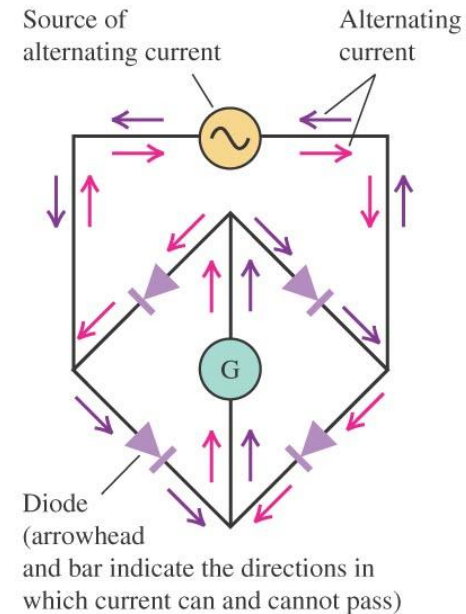

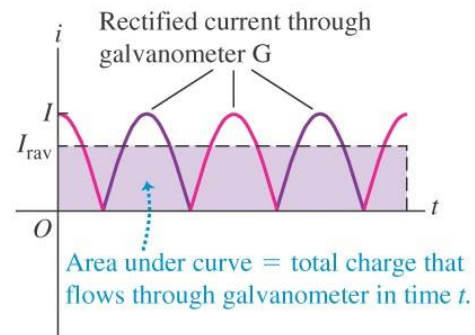(b) Graph of the full-wave rectified current and its average value, the rectified average current I_{rav}




RC Circuit – Exponential Decay

- An RC circuit is a common circuit used in electronic filters
- The basic idea is it takes time to charge a capacitor through a resistor
- Recall that a capacitor C with Voltage V across it has charge $Q=CV$
- Current $I = dQ/dt = C dV/dt$
- In a circuit with a capacitor and resistor in parallel the voltage across the resistor must equal opposite that across the capacitor
- Hence $V_C = -V_R$ or $Q/C = -IR$ or $Q/C + IR = 0$ (note the current I through the resistor must be responsible for the dQ/dt – Kirchoff or charge conservation)
- Now take a time derivative $dQ/dt/C + R dI/dt = I/C + R dI/dt = 0$
- OR $dI/dt + I/RC$ simply first order differential equation
- Solution is $I(t) = I_0 e^{-t/RC} = I_0 e^{-t/\tau}$ where $\tau = RC$ is the “time constant”
- Voltage across resistor $V_R(t) = IR = I_0 R e^{-t/RC} = V_0 e^{-t/RC} = -V_C(t)$ voltage across capacitor
- Note the exponential decay
- We can also write the eq as $R dQ/dt + Q/C = 0$


Discharging a capacitor

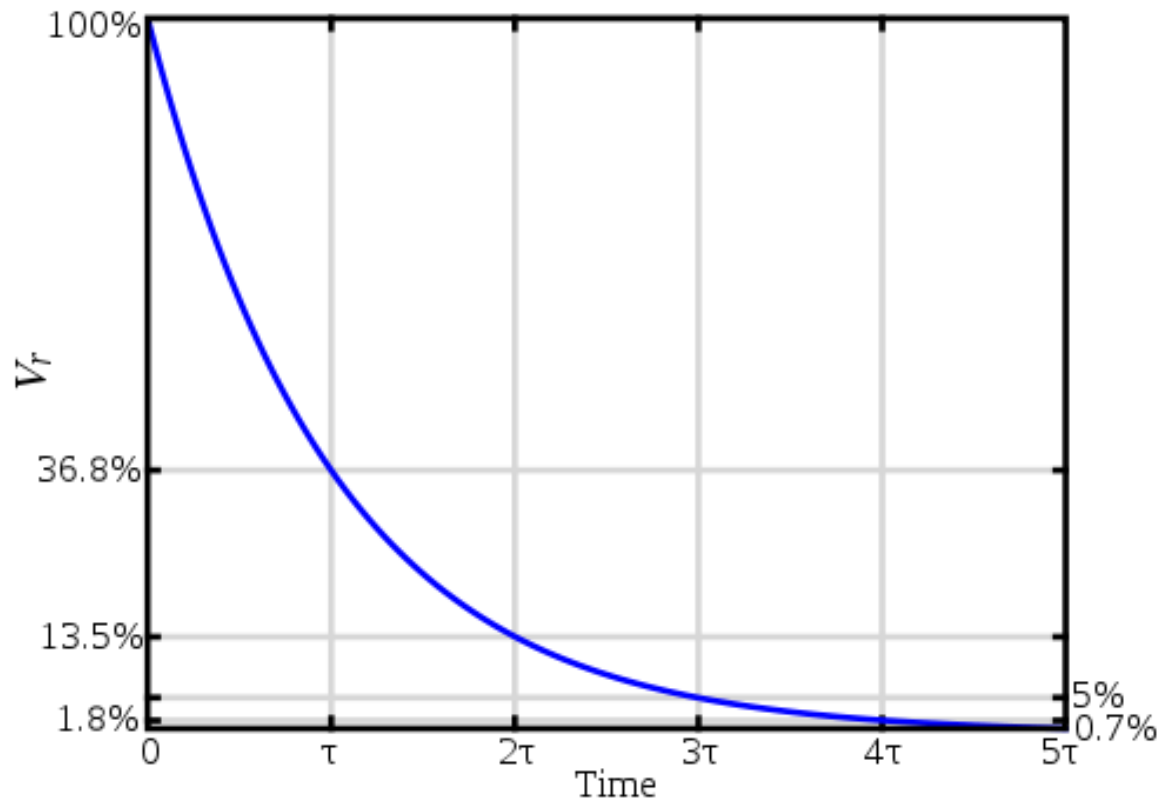- Imagine starting with a capacitor C charged to voltage V_0
- Now discharge it starting at $t=0$ through resistor R
- $V(t) = V_0 e^{-t/RC}$



Charging a Capacitor

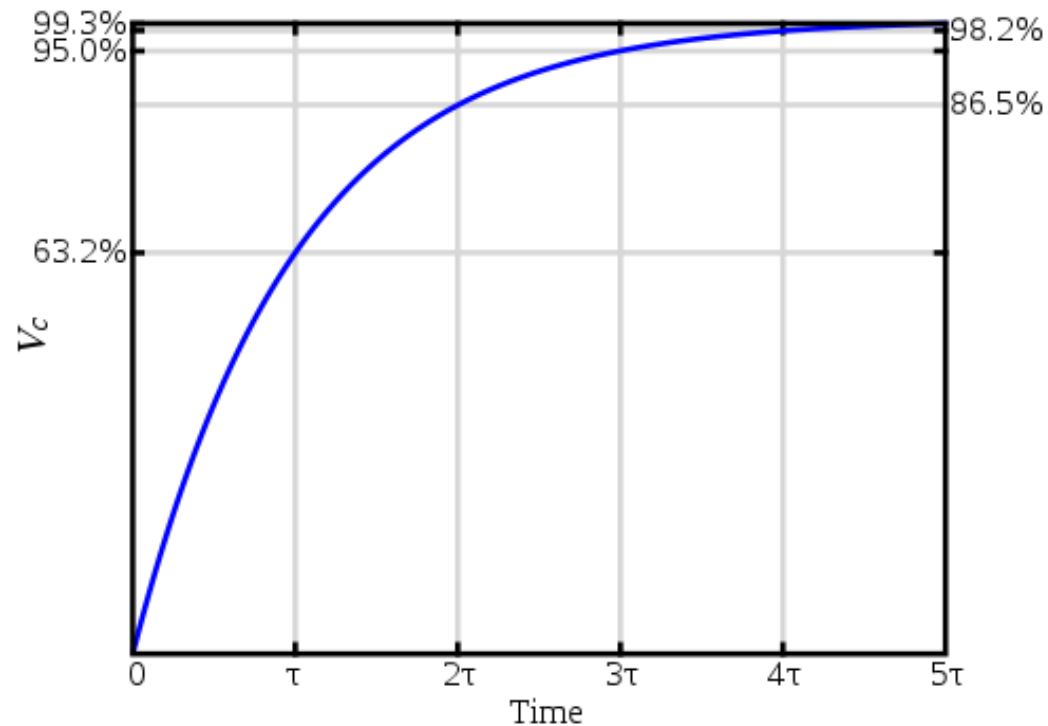- Start with a capacitor C that is discharged (0 volts)
- Now hook up a battery with a resistor R
- Start the charge at $t=0$
- $V(t) = V_0 (1 - e^{-t/RC})$




RC Circuits – Another way

- Lets analyze this another way
- In a closed loop the total EMF is zero (**must be careful here once we get to induced electric fields from changing magnetic fields**)
- In quasi static case $\int \mathbf{E} \cdot d\mathbf{l} = 0$ (voltage sum) over a closed loop
- Charge across the capacitor $Q = CV$ $I = dQ/dt = C dV/dt$
- But the same $I = -V/R$ (minus as V across cap is minus across R if we go in a loop)
- $CdV/dt = -V/R$ or $C dV/dt + V/R = 0$ or $dV/dt + V/RC = 0$
- Solution is $V(t) = V_0 e^{-t/RC}$
- Same solution as before
- The time required to fall from the initial voltage V_0 to V_0/e is time $\tau = RC$

Complex impedances

- Consider the following series circuit
- If we put an input Voltage V_{in} across the system
- We get a differential eq as before but with V_{in}
- $V_{in} + IR + Q/C = 0$ $\int E \cdot dl = 0$ around the closed loop
- $V_{in} + R dQ/dt + Q/C = V_{in} + IR + \int I dt/C$ – we can write the solution as a complex solution $I = I_0 e^{i\omega t}$
- $V_{in} + IR + \int I dt/C$
- We can make this more
- General letting $V_{in} = V_0 e^{i\omega t}$
- This allows a driven osc term – freq ω
- $V_0 e^{i\omega t} + R I_0 e^{i\omega t} + I_0 e^{i\omega t} / (i\omega C)$
- $V_0 + R I_0 + I_0 / (i\omega C)$ - thus we can interpret this as a series of impedances (resistance) Z (general impedance) where $Z_R = R$ is the normal impedance of a resistor and $Z_C = 1/(i\omega C) = -i/(\omega C)$ is the impedance of a capacitor
- Note the impedance of a capacitor is complex and proportional to $1/\omega C$ - the minus i will indicate a 90 degree phase shift

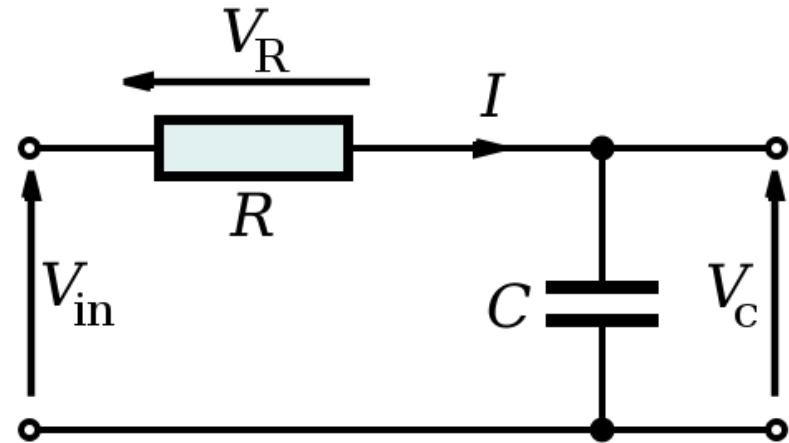


Q26.9

A battery, a capacitor, and a resistor are connected in series. Which of the following affect(s) the maximum charge stored on the capacitor?

- A. the emf \mathcal{E} of the battery
- B. the capacitance C of the capacitor
- C. the resistance R of the resistor
- D. both \mathcal{E} and C
- E. all three of \mathcal{E} , C , and R

A26.9

A battery, a capacitor, and a resistor are connected in series. Which of the following affect(s) the maximum charge stored on the capacitor?

- A. the emf \mathcal{E} of the battery
- B. the capacitance C of the capacitor
- C. the resistance R of the resistor
-  D. both \mathcal{E} and C
- E. all three of \mathcal{E} , C , and R


Q26.10

A battery, a capacitor, and a resistor are connected in series. Which of the following affect(s) the rate at which the capacitor charges?

- A. the emf \mathcal{E} of the battery
- B. the capacitance C of the capacitor
- C. the resistance R of the resistor
- D. both C and R
- E. all three of \mathcal{E} , C , and R


A26.10

A battery, a capacitor, and a resistor are connected in series. Which of the following affect(s) the rate at which the capacitor charges?

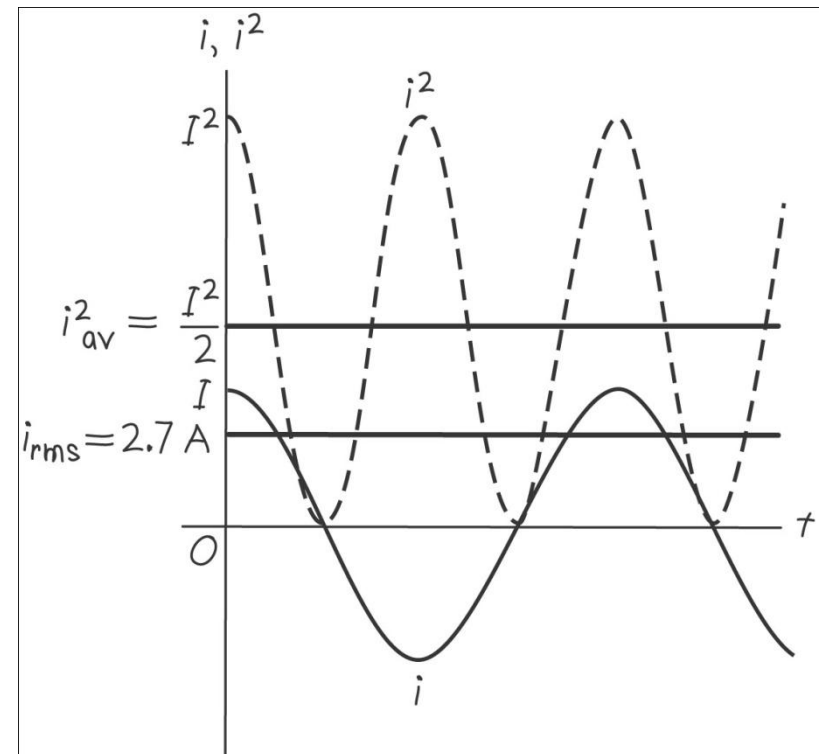- A. the emf \mathcal{E} of the battery
- B. the capacitance C of the capacitor
- C. the resistance R of the resistor
-  D. both C and R
- E. all three of \mathcal{E} , C , and R

Current in the device I'm using right now

- A desktop PC draws current from a plug to the wall, but what are the details?



Power produced by or transferred into a circuit element

$$P = iV$$


Current through the
circuit element

Voltage (absolute value)
across the circuit element



Source of emf: Power flows out of the source and into the moving charges.
Resistor: Power flows out of the charges and into the resistor.

CHAPTER 21: FIGURE 21-4

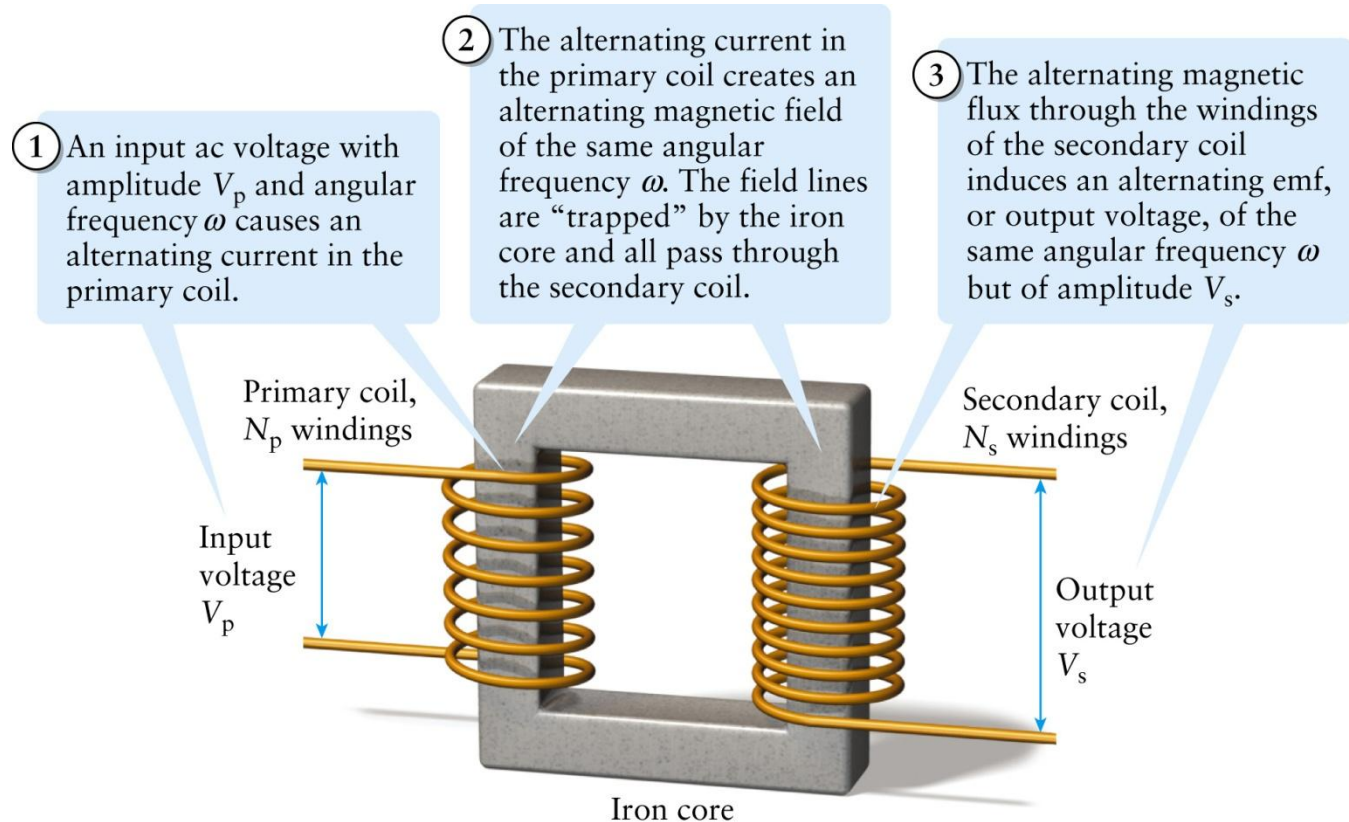

The amplitude V_s of the output voltage equals (N_s/N_p) times the amplitude V_p of the input voltage.

- If $N_s > N_p$, then $V_s > V_p$. This is a step-up transformer.
- If $N_s < N_p$, then $V_s < V_p$. This is a step-down transformer.

Amplitudes of the input (p) and output (s) voltages

$$\frac{V_s}{V_p} = \frac{V_{s,rms}}{V_{p,rms}} = \frac{N_s}{N_p}$$

Number of windings in the primary coil (p) and secondary coil (s)

Rms values of the input (p) and output (s) voltages

Inductance of a coil

Number of windings in the coil

$$L = \frac{N\Phi_B}{i}$$

Magnetic flux through each winding of the coil due to the field produced by the coil itself

Current in the coil

Voltage across an inductor


Inductance of the inductor

$$V = -L \frac{\Delta i}{\Delta t}$$

Rate of change of the current i in the inductor

The negative sign means that the voltage opposes any change in the current.

CHAPTER 21: FIGURE 21-8_2

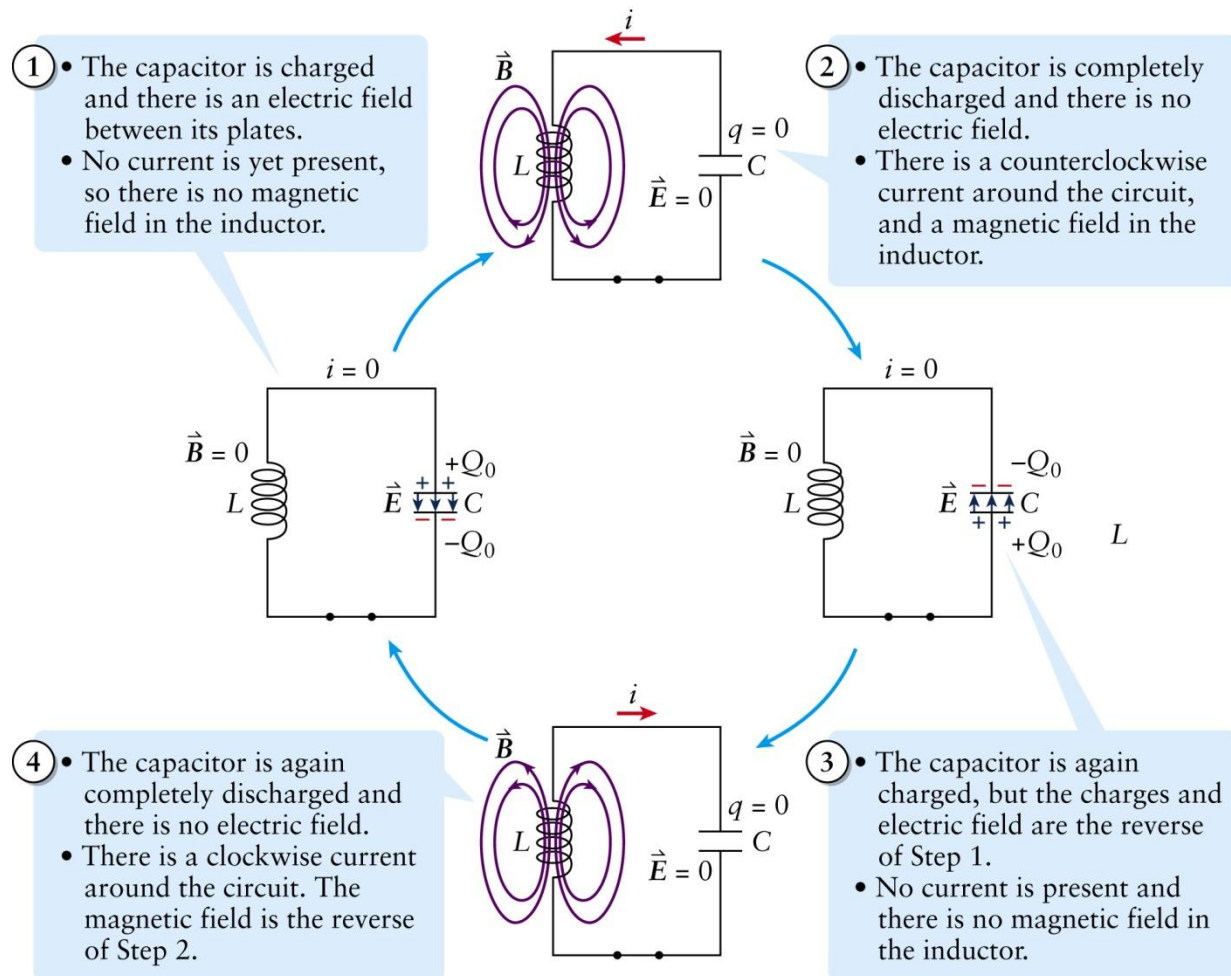

Energy in an
LC circuit

Magnetic energy U_B
in the inductor

Electric energy U_E
in the capacitor

$$E = \frac{1}{2} Li^2 + \frac{q^2}{2C}$$

Charge on the capacitor

Inductance of
the inductor

Current in
the inductor

Capacitance of
the capacitor


Table 21-1 Comparing a block on an ideal spring to an LC circuit

Quantity for a block on an ideal spring	Corresponding quantity for an LC circuit
spring displacement, x	capacitor charge, q
block velocity, $v_x = \Delta x / \Delta t$	current, $i = \Delta q / \Delta t$
spring constant of the spring, k	reciprocal of the capacitance, $1/C$
mass of the block, m	inductance, L
oscillation amplitude, A	maximum capacitor charge, Q_0
potential energy of the spring, $U_{\text{spring}} = \frac{1}{2}kx^2$	electric energy in the capacitor, $U_E = \frac{q^2}{2C}$
kinetic energy of the block, $K = \frac{1}{2}mv_x^2$	magnetic energy in the inductor, $U_B = \frac{1}{2}Li^2$


Resistors in an AC circuit

- Ohm's Law applied in oscillatory fashion.


(a) Circuit with ac source and resistor

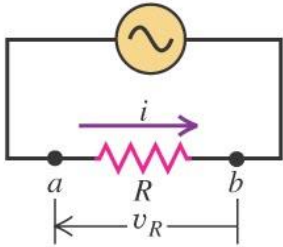

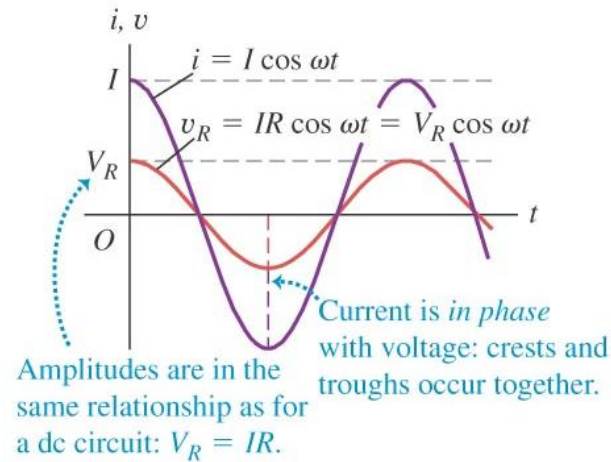(b) Graphs of current and voltage versus time




(c) Phasor diagram

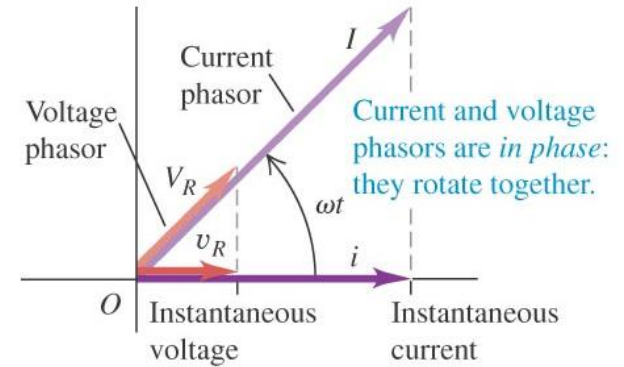


Inductors in an AC circuit

- Replace the resistor in the previous slide with an inductor.

(a) Circuit with ac source and inductor

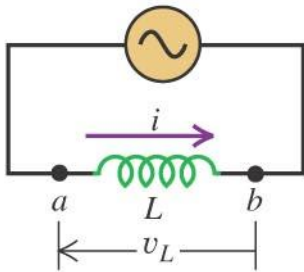


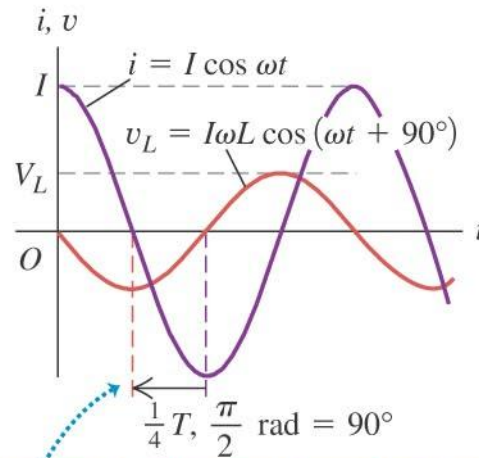(b) Graphs of current and voltage versus time



Voltage curve *leads* current curve by a quarter-cycle (corresponding to $\phi = \pi/2 \text{ rad} = 90^\circ$).

(c) Phasor diagram

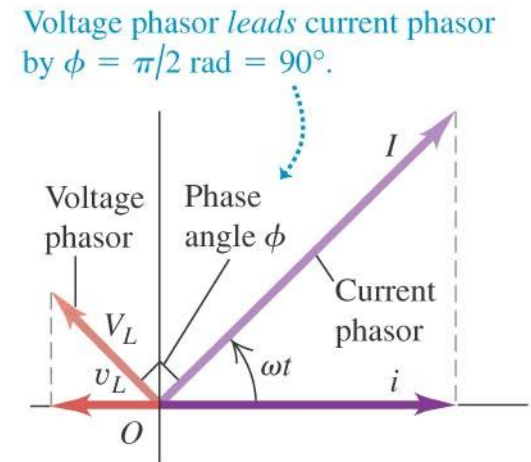


Voltage phasor *leads* current phasor by $\phi = \pi/2 \text{ rad} = 90^\circ$.



Capacitance in an AC circuit

- Because this is a series circuit, the current is the same through the capacitor as through the resistor just considered.


(a) Circuit with ac source and capacitor

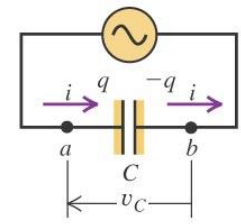

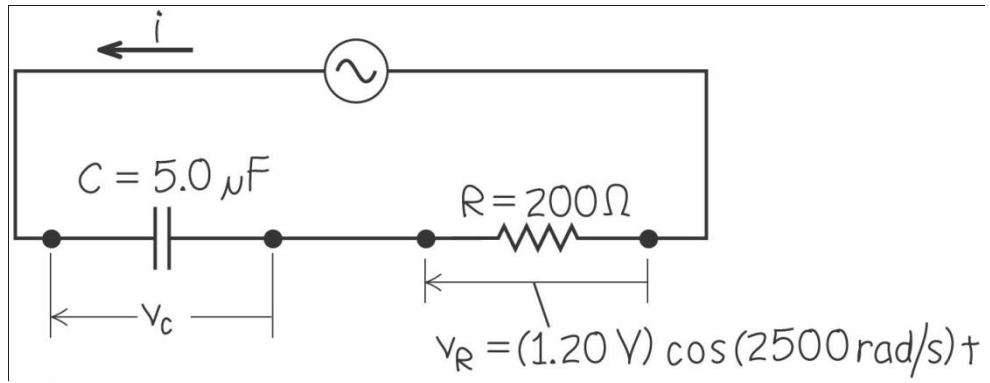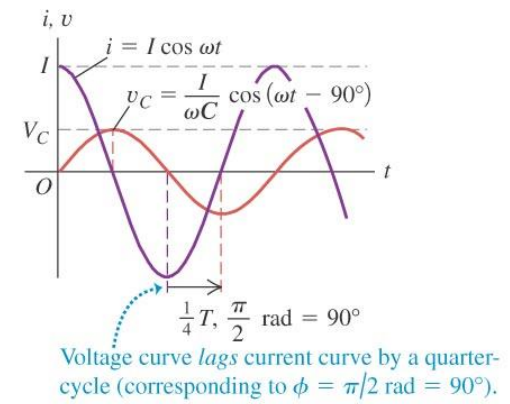(b) Graphs of current and voltage versus time



(c) Phasor diagram

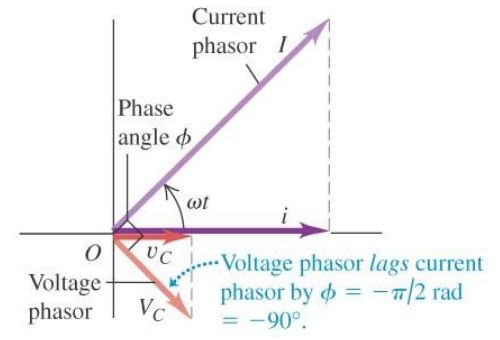

Comparing AC circuit elements

- Summary of circuit elements.
- Frequency dependence of reactance

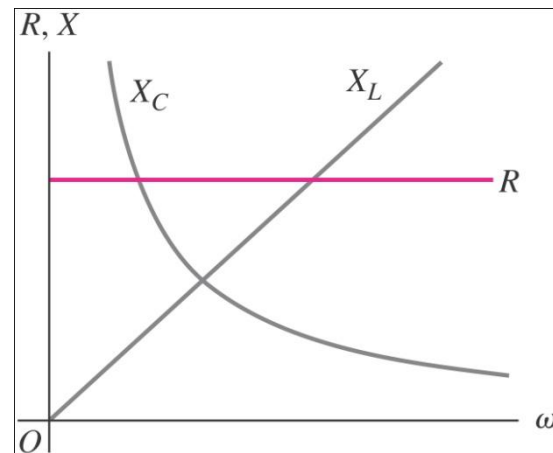



Table 31.1 Circuit Elements with Alternating Current

Circuit Element	Amplitude Relationship	Circuit Quantity	Phase of v
Resistor	$V_R = IR$	R	In phase with i
Inductor	$V_L = IX_L$	$X_L = \omega L$	Leads i by 90°
Capacitor	$V_C = IX_C$	$X_C = 1/\omega C$	Lags i by 90°


The loudspeaker, a useful application

- The woofer (low tones) and the tweeter (high tones) connect in parallel through a “crossover.”

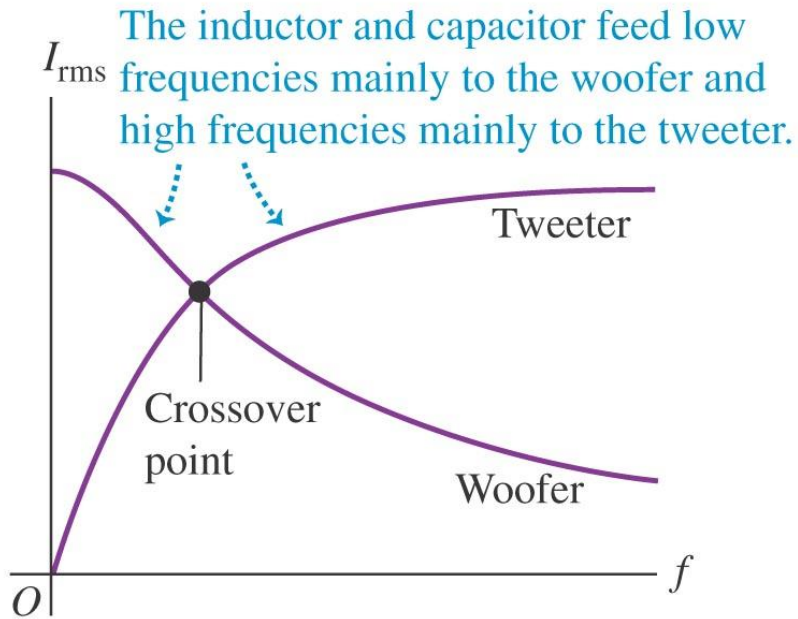Graphs of rms current as functions of frequency for a given amplifier voltage



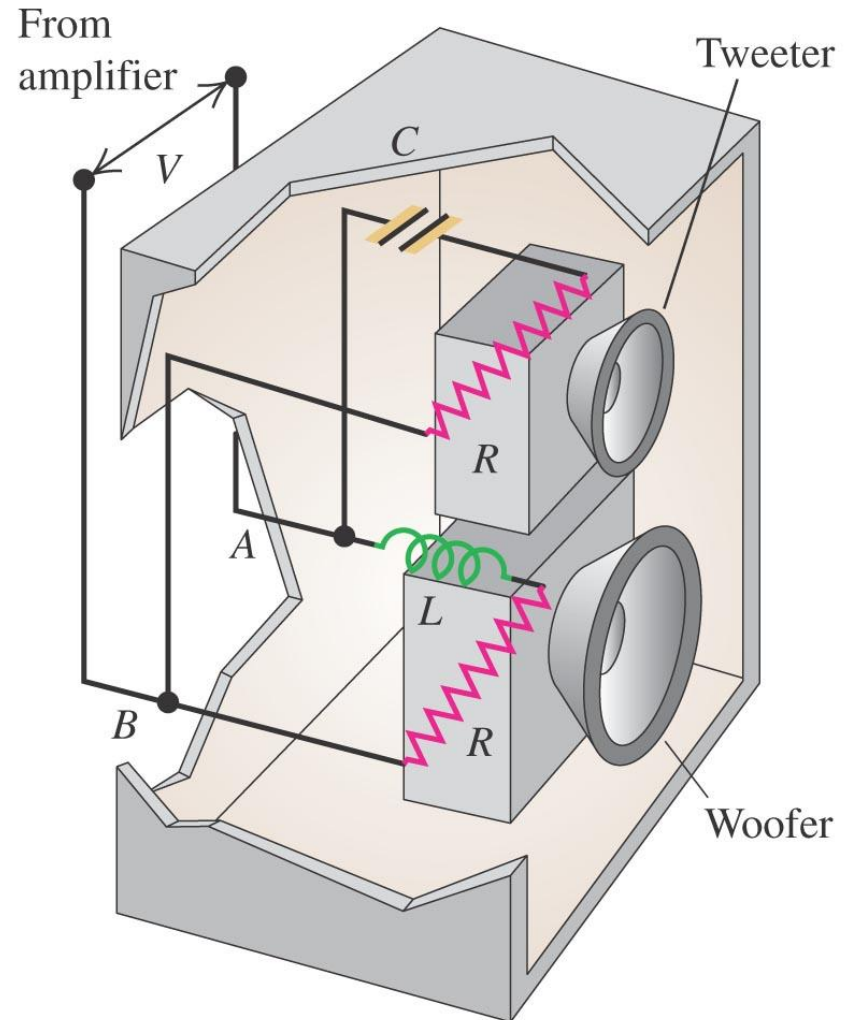
A crossover network in a loudspeaker system




The L-R-C circuit



(a) Series R - L - C circuit

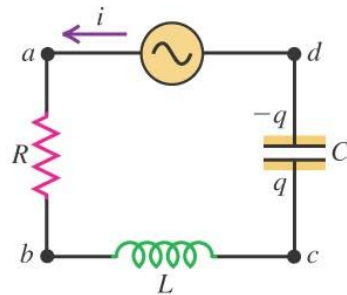


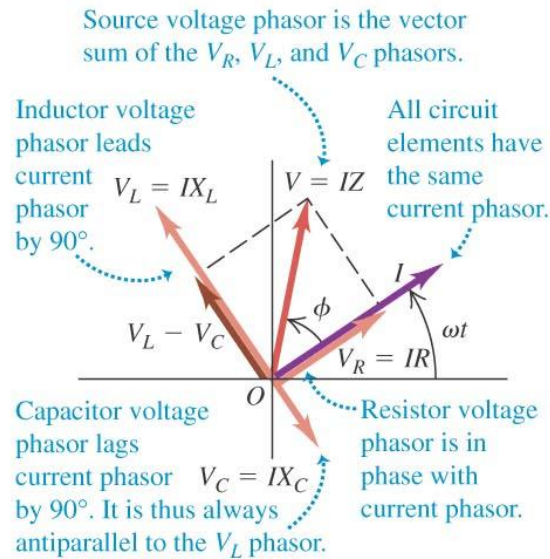(b) Phasor diagram for the case $X_L > X_C$




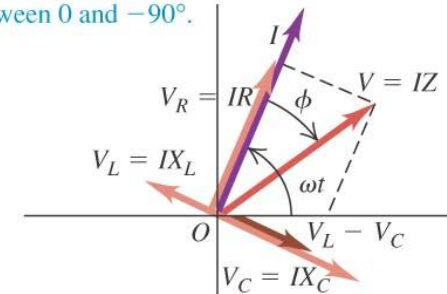(c) Phasor diagram for the case $X_L < X_C$

If $X_L < X_C$, the source voltage phasor lags the current phasor, $X < 0$, and ϕ is a negative angle between 0 and -90° .



An L-R-C circuit II

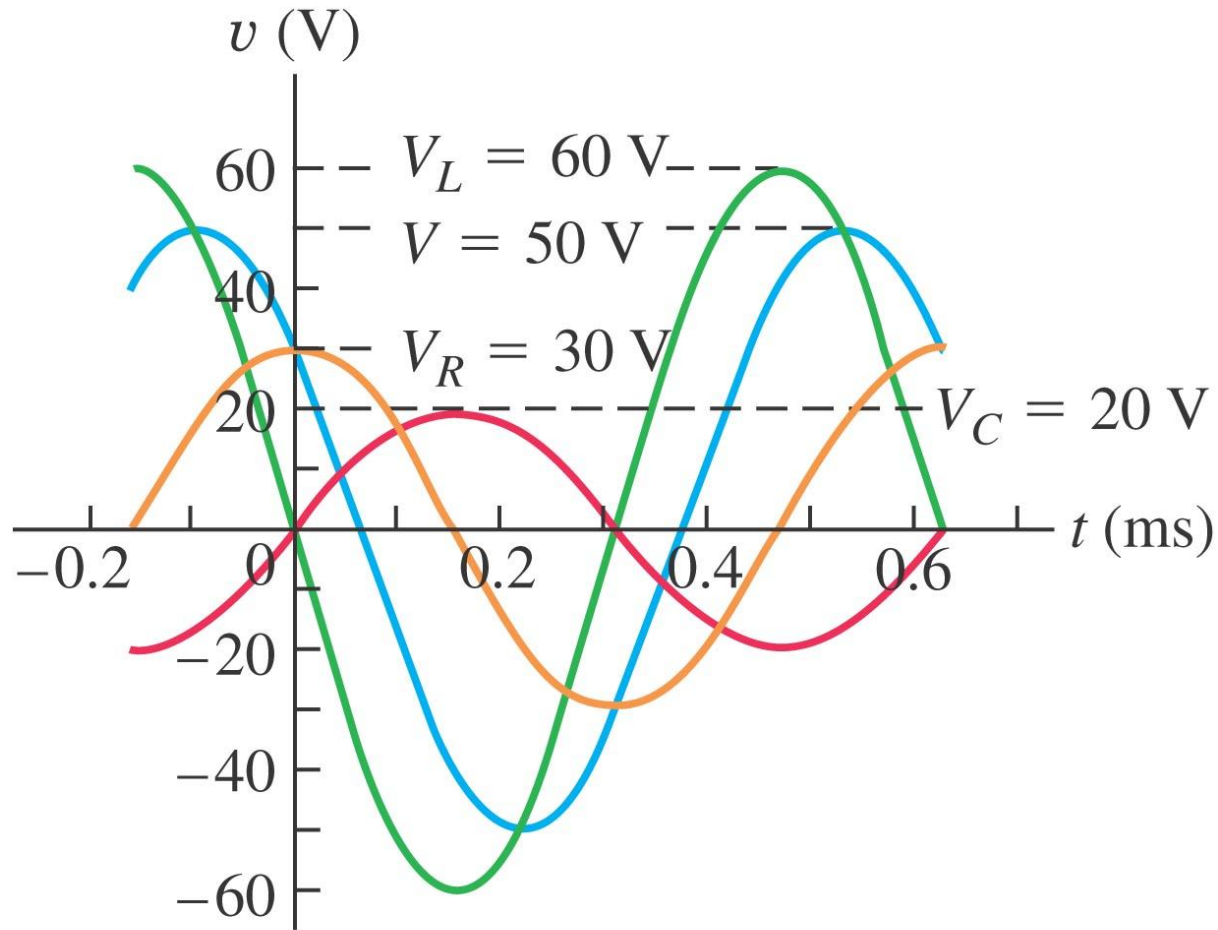


KEY: v — v_R — v_L — v_C —

Power in an inductor

- Consider current, voltage, and power as functions of time.

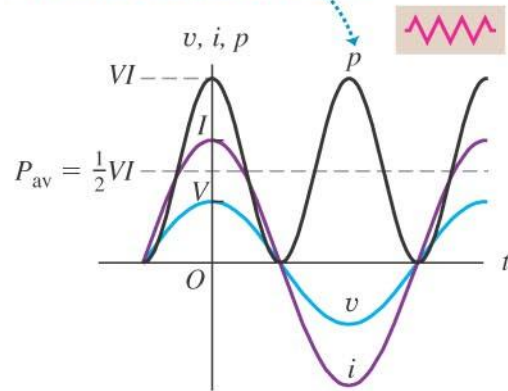
(a) Pure resistor

For a resistor, $p = vi$ is always positive because v and i are either both positive or both negative at any instant.




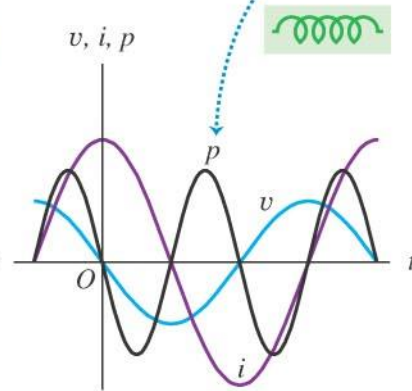(b) Pure inductor

For an inductor or capacitor, $p = vi$ is alternately positive and negative, and the average power is zero.




(c) Pure capacitor

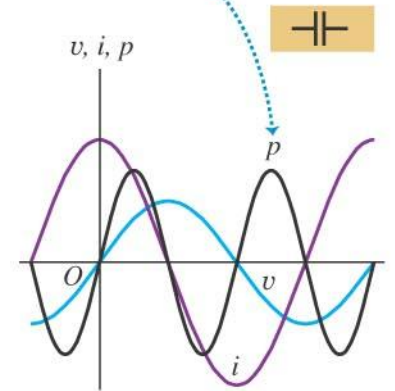

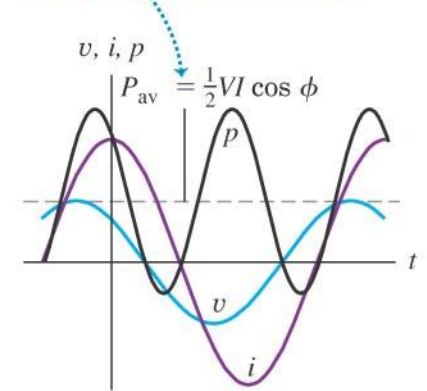(d) Arbitrary ac circuit

For an arbitrary combination of resistors, inductors, and capacitors, the average power is positive.



KEY: Instantaneous current, i —


Instantaneous voltage across device, v —

Instantaneous power input to device, p —


Circuit behavior at resonance

- Look at the maximum I when the impedance is a minimum.

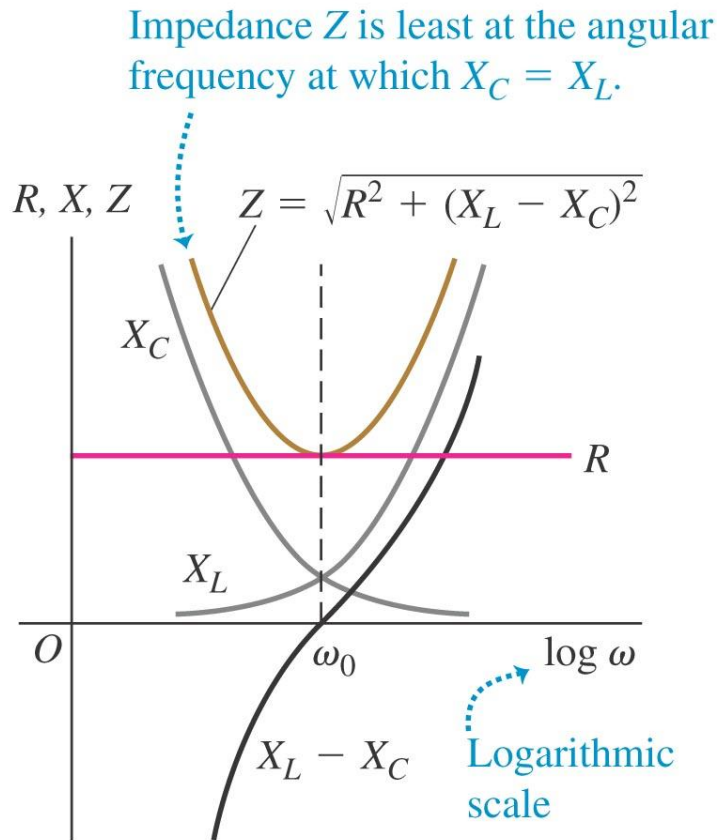Reactance, resistance, and impedance as functions of angular frequency



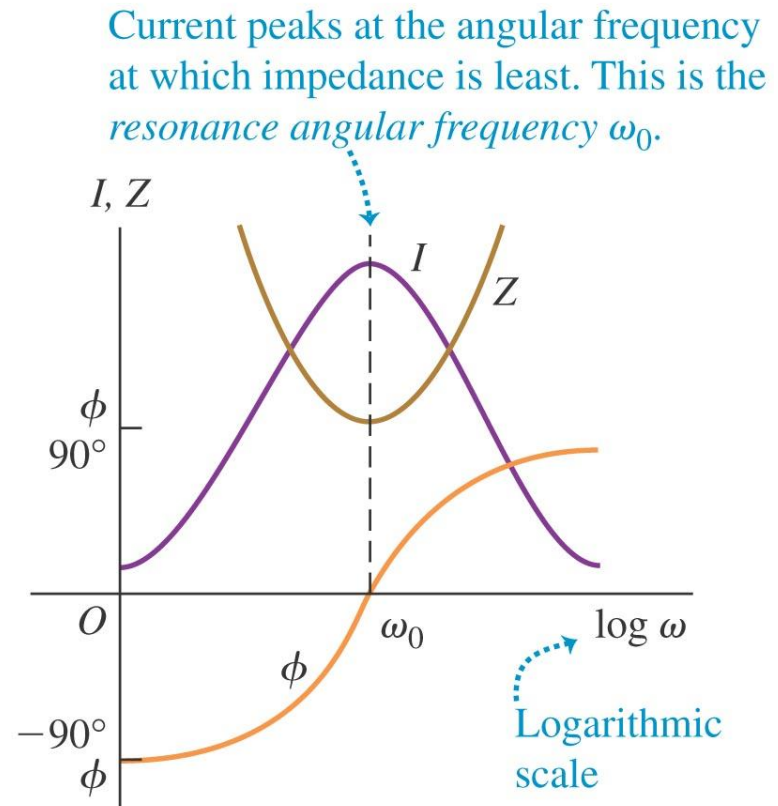Impedance, current, and phase angle as functions of angular frequency



Tuning a radio – LRC circuit – tuned to station – AM/ FM radio

